

# COL215: Digital Logic and System Design

Special Laboratory Semester, AY 2021-22

Department of Computer Science & Engineering

## Lab Assignment 6

### Stopwatch

#### Learning Objective:

Learn (i) use of a pre-designed circuit (4-digit display, in this case) as a building block, (ii) creation of time reference.

#### Specifications:

Design a stopwatch and implement it on BASYS 3 board, using its 7-segment display and push buttons. Since the display has only 4 digits, assign these as follows - 1 digit for minutes, two digits for seconds and one digit for tenths of a second. Use three push buttons as follows.

- Start/Continue • Pause • Reset

#### Details:

The circuit will consist of a few counters, time reference and display (from previous assignment).

- A. Counters: The design will be centered around an ensemble of four counters described below.
- A modulo 10 counter to count tenths of a second
  - A modulo 10 counter to count unit digits of seconds
  - A modulo 6 counter to count tens of seconds
  - A modulo 10 counter to count minutes

The ensemble is driven by a 10 Hz timing reference. Provide for an enable input and a reset input. The enable input comes from a flip-flop/latch that is set to '1' when Start/Continue button is pressed and set to '0' when Pause button is pressed. Reset input comes from a push button.

The counters can be synchronous or asynchronous. In asynchronous counters, various bits may not change simultaneously, but the time delays will not be perceptible to the eye.

- B. Time reference: 100 MHz clock available on BASYS 3 board needs to be divided by  $10^7$  to get 10 Hz clock that updates tenths of a second. Note that a modulo N counter divides frequency by N. Recall that the display requires a clock in the range of 250 Hz to 4 kHz. Suppose you use 1 kHz clock for the display. Then you can first divide 100 MHz frequency by  $10^5$  to get 1 kHz and then divide it by 100 to get 10 Hz.

Create an appropriate constraint file for connecting the circuit to on-board resources - slide switches, 7-segment displays and clock.